



# PSCAD Cookbook

## Reactor Switching Study

### Manitoba HVDC Research Centre

a division of Manitoba Hydro International Ltd.

211 Commerce Drive

Winnipeg, MB R3P 1A3, Canada

[www.hvdc.ca](http://www.hvdc.ca)

Written for v4.5  
Initial, June 1, 2013

## Contents

<b>8. REACTOR SWITCHING STUDY .....</b>	<b>1</b>
8.1 REACTOR SWITCHING STUDY .....	1

## 8. Reactor Switching Study

### 8.1 Reactor Switching Study

#### Motivation

This case is used to illustrate the effects of reactor switching. A system becomes isolated into two parts when a breaker interrupts the current to a reactor. The two isolated parts of the system oscillate at their respective natural frequencies. Since the stray capacitances are typically very small, high natural frequencies are possible. This is likely to impose a fast rising voltage transient across the circuit breaker (TRV). This can pose problems to the circuit breaker and cause restrike of the arc that is being interrupted.

#### System Overview

Figure 1 illustrates the circuit under consideration. This figure models a power system connected to a reactor through a breaker. Here the voltage source and inductor  $L_1$  together form the Thevenin equivalent circuit model of the power system, and  $L_2$  models the innate inductive impedance of the reactor. Capacitors  $C_1$  and  $C_2$  account for the stray capacitance of a transformer winding (connected to the power system) and the reactor winding, respectively. Also, the resistor  $R$  accounts for the reactor winding loss. The breaker is used to interrupt the current to the reactor, isolating the two systems.

This essentially is the situation of a normal reactor switching (possibly to regulate the voltage on the 138 kV (3  $\phi$ ) bus).

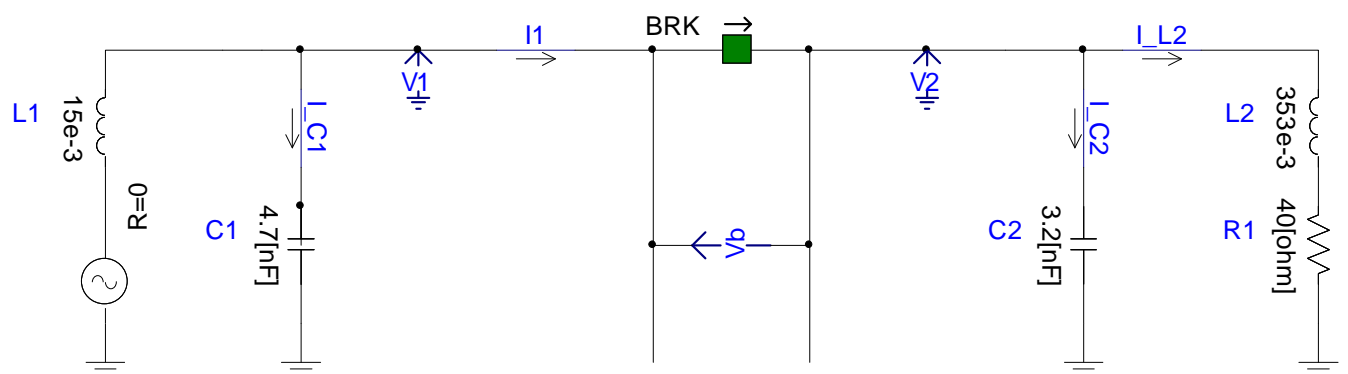


Figure 1: System Circuit Diagram

## Simulation Results

Note the voltage appearing across the breaker immediately following the current interruption (Figure 2 and Figure 3). The voltage across the breaker ( $V_b$ ) plays an important role in determining if the breaker will interrupt the circuit successfully.  $V_b$  is commonly referred to as the 'transient recovery voltage' or TRV.

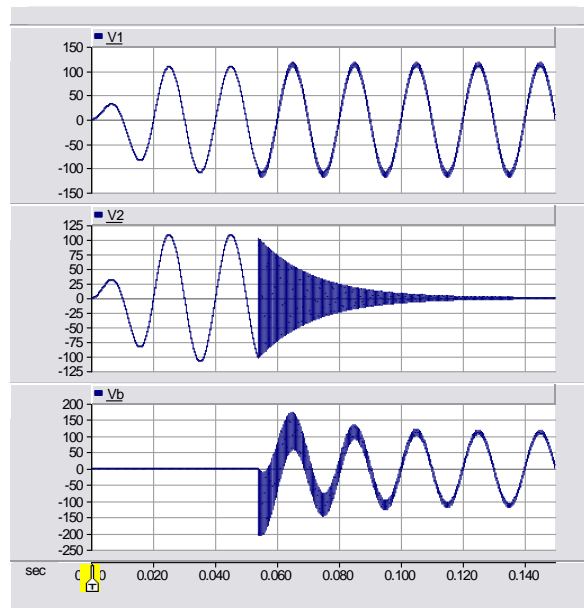


Figure 2: Response of the System to Breaker Opening

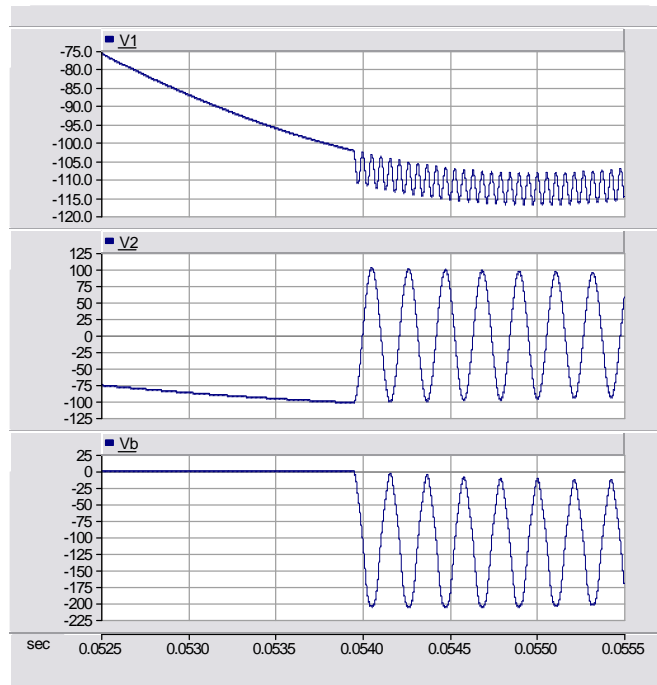


Figure 3: Response of the System to Breaker Opening (a Closer View)

With the breaker open, both systems form second order circuits with resonant a frequency  $f_o = \frac{1}{2\pi\sqrt{LC}}$ . The power system side has  $f_{o1} = 19 \text{ kHz}$  ( $T_{o1} = 53 \mu\text{s}$ ) while the reactor side has  $f_{o2} = 4.7 \text{ kHz}$  ( $T_{o2} = 212.8 \mu\text{s}$ ). Figure 4 displays the results of the PSCAD simulation for the circuits; the results are consistent with the theoretical values.

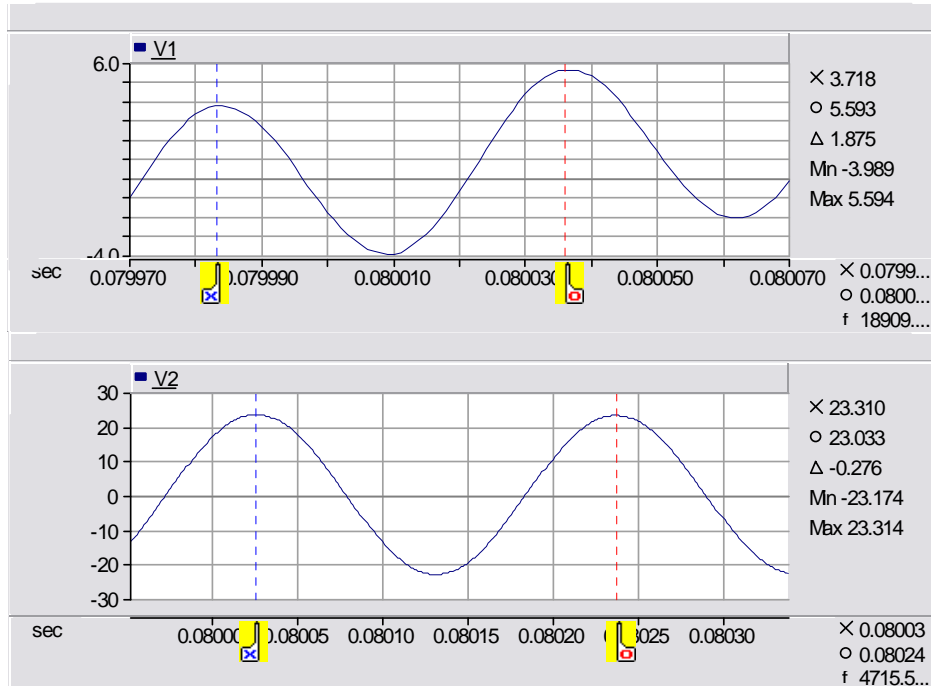


Figure 4: Systems Oscillating at their Respective Natural Frequencies

### Notable Features

The following are notable features of this model:

- The Voltage  $v_b$  is the 'transient recovery voltage' TRV.
- The maximum TRV peak possible is twice the value of the input voltage.

### PSCAD

Refer to PSCAD case: *Reactor\_Switching.pscx*

DOCUMENT TRACKING

Rev.	Description	Date
<b>0</b>	Initial	01/Jun/2013